

University of Illinois at Urbana-Champaign
Dept. of Electrical and Computer Engineering

ECE 120: Introduction to Computing

Building with Abstraction and a First Example

Optimization at the Level of Gates is Always Possible

One can always solve a problem by

- developing complete Boolean expressions,
- solving for “good” forms with K-maps (or algebra, with more variables),
- implementing the resulting equations,
- tuning logic to reduce gate sizes (number of inputs) and fanout (the number of gates using a single gate’s output).

You can now perform such a process.

But Optimization at Gate Level is Rarely Needed

Such detail is rarely needed for a satisfactory solution.

Instead, humans can

- use abstraction and build with components such as adders and comparators, or
- use extra levels of logic to describe functions more intuitively.

Computer-aided design (CAD) tools

- can help with low-level optimizations.
- In many cases, CAD tools can do better than humans because they explore more options.

Tradeoffs are Always Made in Some Context

Context is important!

If a mechanical engineer produces a 0.5% boost in efficiency for internal combustion engines sized for automobiles, that engineer will probably win a major prize.

In our field, engineers spend a lot of time

- improving the designs of arithmetic units and memory, and
- improving CAD tools’ ability to optimize.

But Optimization at Gate Level is Rarely Needed

“Premature optimization is the root of all evil.”
– Sir C.A.R. “Tony” Hoare

Don't spend time optimizing

- something that is likely to change, nor
- something that does not contribute much to the overall system goodness (any metric).

The flip side:

- don't ignore scaling issues when choosing algorithms, and
- don't design in a way that prohibits/inhibits optimization.

First Example: Subtraction

Let's start with something simple.

Let's build a subtractor.

How do we subtract as humans?

Example: Subtraction of 5-Digit Numbers

Let's do an example with **5-digit numbers**

$$\begin{array}{r} 12345 \\ - \quad 871 \\ \hline \end{array}$$

Negate by finding the “9's complement” and adding 1.

Example: Subtraction of 5-Digit Numbers

Let's do an example with **5-digit numbers**

$$\begin{array}{r} \text{We have no } \textcircled{0}1 \quad 1 \\ \text{space for} \quad 12345 \\ \text{that digit!} \quad + \quad 99129 \\ \hline 11474 \end{array}$$

Good, we got the right answer
(12345 – 871 = 11474)!

Use an Adder to Implement a Subtractor

Ok, maybe your elementary school taught subtraction a different way.

But you probably did use that approach in your ECE120 homework to subtract **unsigned** and **2's complement** values.

$$A - B = A + (\text{NOT } B) + 1$$

(where "NOT" applies to all bits of **B**)

Instead of mimicking the human subtraction process, let's use an adder to implement a subtractor...


Use an Adder to Implement a Subtractor

Take a look at the design to the right.

The core is an **N-bit adder**.

We want to calculate the difference **$D = A - B$** .

 We **modify the inputs slightly** to perform the subtraction.




Convert B to its 1's Complement

The input **A** is unchanged.

The input **B** is transformed to its 1's complement.

How do we implement 1's complement?

N inverters!

 


With $C_{in} = 1$, the Adder Produces $A - B$

Finally, the C_{in} input is set to 1.

So what does the adder calculate?

$$A + (\text{NOT } B) + 1$$

which is **$A - B$** , as desired.

 


Calculate D to Understand the Carry Out Signal

What does the carry out C_{out} mean?

Remember that the 1's complement is $(2^N - 1) - B$.

 So we obtain D
 $= A + (2^N - 1) - B + 1$
 $= A - B + 2^N$



Carry Out Signal (Opposite Sense) Still Means Overflow


So $D = A - B + 2^N$.

But C_{out} is the 2^N term from the adder.

Thus

- $C_{out} = 1$ means $A \geq B$
- $C_{out} = 0$ means $A < B$

 So for unsigned subtraction $C_{out} = 0$ indicates overflow!



Carry Out Signal (Opposite Sense) Still Means Overflow

What if we want a device that does both addition and subtraction?

We need a way to choose the operation.

Add a control signal S

- $S = 0$: addition
- $S = 1$: subtraction

And the modify the adder inputs with S

- A ... **unmodified**
- B ... **$B \text{ XOR } S$** (bitwise)
- C_{in} ... S