

University of Illinois at Urbana-Champaign  
Dept. of Electrical and Computer Engineering

## ECE 120: Introduction to Computing

Another Example of Serialization:  
Power-of-2 Checker

## Review of General Bit-Slice Model

### General model parameters


**N-bit** operands

**P** bits of input from operands

**Q** bits of output produced

**M** bits between bit slices

 **R** bits of final output (not shown; produced by output logic operating on **M** bits from last bit slice).



## Parameter Values for a Power-of-2 Checker

### Power-of-2 checker parameters


**N-bit** operands

**P = 2**

**Q = 0**

**M = 2**

**R = 1**

 

## Initialization of a Power-of-2 Checker


Our power-of-2 checker bit slice uses the representation shown here to pass information between slices.

What values should be passed to the first bit slice?

No 1 bits yet, so  $C_1 C_0 = 00$

| $C_1$ | $C_0$ | meaning    |
|-------|-------|------------|
| 0     | 0     | no 1 bits  |
| 0     | 1     | one 1 bit  |
| 1     | 0     | not used   |
| 1     | 1     | >one 1 bit |

### Example: A Power-of-2 Checker

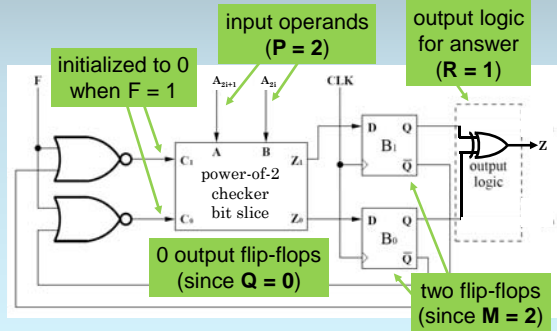

### Discrete Time Implies Delayed Results: N = 8

yellow = inputs (green = bit slice labels)

| cycle # | F | A | B | B <sub>1</sub> | B <sub>0</sub> | C <sub>1</sub> | C <sub>0</sub> | Z <sub>1</sub> | Z <sub>0</sub> |
|---------|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|
| 0       | 1 | 0 | 0 | bits           | bits           | 0              | 0              | 0              | 0              |
| 1       | 0 | 0 | 1 | 0              | 0              | 0              | 0              | 0              | 1              |
| 2       | 0 | 0 | 0 | 0              | 1              | 0              | 1              | 0              | 1              |
| 3       | 0 | 1 | 0 | 0              | 1              | 0              | 1              | 1              | 1              |
| 4       | x | x | x | 1              | 1              | ?              | ?              | ?              | ?              |

blue = outputs     $Z = B_1 \oplus B_0 = 0$

### A Power-of-2 Checker Consists of Four Parts

Let's analyze the area of a power-of-2 checker.

We have:


- one bit slice,
- two flip-flops,
- two 2-input NOR gates (selection logic),
- and a 2-input XOR.

16 2-input gates and four inverters
 
### A Power-of-2 Checker Contains One Bit Slice

Here's our design for the power-of-2 checker bit slice.

So we need **three 2-input gates** and **two 3-input gates**.



## A Power-of-2 Checker Consists of Four Parts

Let's analyze the area of a power-of-2 checker.

We have:

- one bit slice, **three 2-input gates and two 3-input gates**
- two flip-flops, **16 2-input gates and four inverters**
- two 2-input NOR gates (selection logic),
- and a 2-input XOR.

Total:  $3+16+2 = 21$  **2-input gates**,  
 $2 = 2$  **3-input gates**,  
 $4 = 4$  **inverters**, and  
 $1$  **2-input XOR**.

## Serial Design is Smaller for $N \geq 10$

To handle **N-bit** operands (2 bits per bit slice), a bit-sliced design requires:

- $3N/2$  **2-input gates** ( $6N$  transistors),
- $N$  **3-input gates** ( $6N$  transistors), and
- **1 2-input XOR**.


A serial design (independent of **N**) requires

- **21 2-input gates** (84 transistors),
- **2 3-input gates** (12 transistors),
- **4 inverters** (8 transistors), and
- **1 2-input XOR**.

**The serial design is smaller for  $N \geq 10$ .**
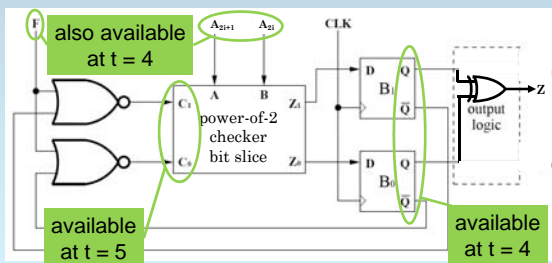
## When Are Inputs Available?


A rising edge arrives at  $t = 0$  (gate delays).



## Delay Analysis for the Bit Slice


And delay?

**2 on all paths.**

 
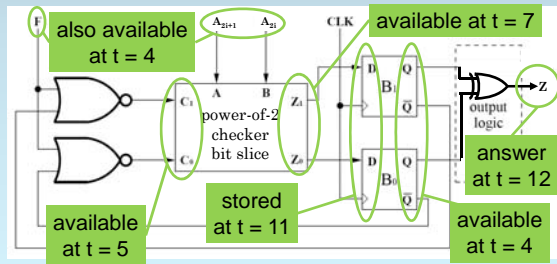
## When Are Results Stored?

A rising edge arrives at  $t = 0$  (gate delays).



## Serial Design is At Least 5.5x Slower

To handle **N-bit** operands, a bit-sliced design requires  **$N + 1$  gate delays**.

For a serial design,

- the clock cycle must be **at least 11 gate delays**, and
- we must execute for  **$N/2$  cycles**, so
- N-bit** operands require **at least  $11N/2$  gate delays**.

**The serial design is at least ~5.5x slower.**

(And may be even slower!)