

University of Illinois at Urbana-Champaign
Dept. of Electrical and Computer Engineering

ECE 120: Introduction to Computing

Finite State Machines (FSMs)

A Finite State Machine (FSM) Models a System

A model of a system

- system moves among a finite set of states
- motion based on external inputs
- produces external outputs

Examples include:

- coin/bill-operated machines,
- many vehicle control systems, and
- computers executing programs.

An FSM Consists of Five Parts

1. a finite set of states (**bits**)
2. a set of possible inputs (**bits**)
3. a set of possible outputs (**bits**)
4. a set of transition rules (**Boolean expressions**)
5. methods for calculating outputs (**Bool. expr's**)

When implemented as a digital system, all parts of an FSM must be mapped to ... **bits!**

A Digital FSM Must be Complete

We implement FSMs as clocked synchronous sequential circuits. (So state ID bits are stored in flip-flops.)

Given **any state** and **any combination of inputs**, a **transition rule** from the given state to a next state **must be defined**.

Self-loops—transitions from a state to itself—are acceptable.

Use Keyless Entry as a Motivating Example

| meaning | state | driver's door | other doors | alarm on? |
|----------------------|----------|---------------|-------------|-----------|
| vehicle locked | LOCKED | locked | locked | no |
| driver door unlocked | DRIVER | unlocked | locked | no |
| all doors unlocked | UNLOCKED | unlocked | unlocked | no |
| alarm sounding | ALARM | locked | locked | yes |

Table is a **list of abstract states**.

A List of Abstract States Need Only List States

In a list of abstract states,

- we can just list the states.
- Adding human meanings is optional (good to have if state names are generic).

Including outputs

- is also optional,
- and implies that **outputs depend only on state**.*

*An extra assumption that we will always make in our class.

An Abstract Next-State Table Captures Expected Behavior

To specify transitions, we use a **next-state table**, which maps combinations of states and inputs into next states.

This is an **abstract next-state table**.

| state | action/input | next state |
|--------|---------------|------------|
| LOCKED | push "unlock" | DRIVER |
| DRIVER | push "unlock" | UNLOCKED |
| (any) | push "lock" | LOCKED |
| (any) | push "panic" | ALARM |

Abstract Next-State Table Does Not Answer All Questions

We wrote transitions for typical use cases, but **the table can be incomplete, ambiguous, and even inconsistent**.

For example, what happens if the user pushes "lock" and "unlock" at the same time?

| state | action/input | next state |
|--------|---------------|------------|
| LOCKED | push "unlock" | DRIVER |
| DRIVER | push "unlock" | UNLOCKED |
| (any) | push "lock" | LOCKED |
| (any) | push "panic" | ALARM |

Many Design Decisions are Usually Needed


All such **design decision** questions should **eventually be considered, and preferably answered.**

Be aware: **any digital logic implementation will define answers.**

Only when any possible answer is acceptable should you make use of “don’t cares.”

Typically, you should **review the final implementation** to determine how any questions left open are answered.

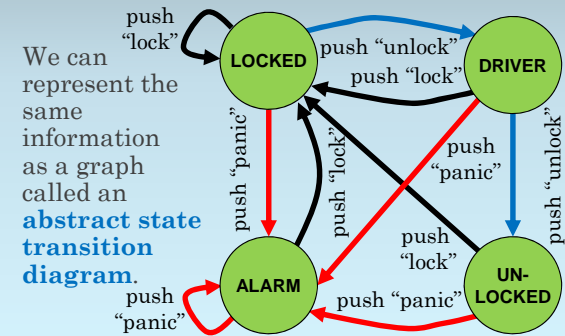Abstract State Transition Diagram: the Same Information



It's Time to Make Our Design Complete and Concrete

The abstract next-state table and the abstract state transition diagram (can) **contain exactly the same information.**

They answer the same questions.

And **neither is complete.**

So. It's time for ... **bits!**

Let's Start with the State Identifiers

How many bits do we need to identify a state?

There are 4 states.

$$\lceil \log_2(4) \rceil = 2 \text{ bits.}$$

Call them S_1S_0 .

“S” is for “S(tate).”

All Outputs and Inputs Must Also Use Bits

What about outputs?

- D** driver door; 1 means unlocked
- R** remaining doors; 1 means unlocked
- A** alarm; 1 means alarm is sounding

And inputs?

- U** unlock button; 1 means it's been pressed
- L** lock button; 1 means it's been pressed
- P** panic button; 1 means it's been pressed

We Next Choose a Representation for States

Now we can choose a representation for states and rewrite our list of states.

The order of states in the list doesn't matter.

| meaning | state | S_1S_0 | D | R | A |
|----------------------|----------|----------|---|---|---|
| vehicle locked | LOCKED | 00 | 0 | 0 | 0 |
| driver door unlocked | DRIVER | 10 | 1 | 0 | 0 |
| all doors unlocked | UNLOCKED | 11 | 1 | 1 | 0 |
| alarm sounding | ALARM | 01 | 0 | 0 | 1 |

Choice of Representation Affects Amount of Logic Needed

As you may realize

- from your experience with bit-sliced designs,
- **the representation does matter** (for the amount of logic needed).

We will talk more later about ways to choose.

Use $S_1^+S_0^+$ to Denote the Next State (in Next Clock Cycle)

The +'s in $S_1^+S_0^+$ indicate that these are values **in the next clock cycle**.

Let's rewrite the next-state table with bits.

- The table gives us $S_1^+S_0^+$ as a function of current state S_1S_0 and inputs **ULP**.
- Such tables typically use binary order for states (vertical) and inputs (horizontal).
- We use Grey code order on both axes for convenience (in copying to K-maps).

How to Fill in the Next-State Table

Where should we start?

| current state S_1S_0 | ULP | | | | | | | |
|---------------------------|-----|-----|-----|-----|-----|-----|-----|-----|
| S_1S_0 | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00 | | | | | | | | |
| 01 | | | | | | | | |
| 11 | | | | | | | | |
| 10 | | | | | | | | |

What about multiple buttons?

Let's make some design decisions first...

Completing the Design Requires Decisions

To fill in the next-state table

- starting with only the abstract design,
- we **need to make many design decisions**,
- including some that we haven't even recognized yet.

For example,

- What happens when the user presses more than one button?
- What happens when the user presses "unlock" in the **UNLOCKED** state?

Make Design Decisions Early When Possible

Let's try to **make decisions first**.

Design decisions can shape the design, and **may conflict with one another**.

Making decisions early and writing them down ensures that

- any **issues are raised early**, and that
- **known decisions are not overlooked**
- (in which case the final design answers them implicitly, with no human guidance).

Start by Deciding How to Handle Multiple Buttons

We're going to start by **prioritizing the buttons**.

Our rules:

- Panic has priority!
- Lock has second priority.
- Unlock only matters when neither of the others is pressed.

Start with the Panic Button (Highest Priority)

The next-state table gives us $S_1^+S_0^+$.

| current state S_1S_0 | ULP | | | | | | | |
|------------------------|-----|-----|-----|-----|-----|-----|-----|-----|
| | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00 | 01 | 01 | | | 01 | 01 | | |
| 01 | 01 | 01 | | | 01 | 01 | | |
| 11 | 01 | 01 | | | 01 | 01 | | |
| 10 | 01 | 01 | | | 01 | 01 | | |

panic button pushed

Continue with the Lock Button (Second Priority)

The next-state table gives us $S_1^+S_0^+$.

| current state S_1S_0 | ULP | | | | | | | |
|------------------------|-----|-----|-----|-----|-----|-----|-----|-----|
| | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00 | 01 | 01 | 00 | 00 | 01 | 01 | | |
| 01 | 01 | 01 | 00 | 00 | 01 | 01 | | |
| 11 | 01 | 01 | 00 | 00 | 01 | 01 | | |
| 10 | 01 | 01 | 00 | 00 | 01 | 01 | | |

lock button pushed

No Buttons? No Change. All Self-Loops

What if the user pushes nothing?

| current state S_1S_0 | ULP | | | | | | | |
|------------------------|-----|-----|-----|-----|-----|-----|-----|-----|
| | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00 | 00 | 01 | 01 | 00 | 00 | 01 | 01 | |
| 01 | 01 | 01 | 01 | 00 | 00 | 01 | 01 | |
| 11 | 11 | 01 | 01 | 00 | 00 | 01 | 01 | |
| 10 | 10 | 01 | 01 | 00 | 00 | 01 | 01 | |

no buttons pushed

Finally, Unlock ... But are We Done?

Two transitions were defined for Unlock.

| current state S_1S_0 | ULP from LOCKED | | | | | | | |
|------------------------|-----------------|-----|-----|-----|-----|-----|-----|-----|
| | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00 | 00 | 01 | 01 | 00 | 00 | 01 | 01 | 10 |
| 01 | 01 | 01 | 01 | 00 | 00 | | | |
| 11 | 11 | 01 | 01 | 00 | 00 | | | |
| 10 | 10 | 01 | 01 | 00 | 00 | 01 | 01 | 11 |

What about these?

from DRIVER

We Have More Design Decisions to Make!

What should happen if we press “unlock” when the car is already fully unlocked (in the **UNLOCKED** state)?

Maybe just stay **UNLOCKED**.

What should happen if we press “unlock” while the alarm is sounding?

- Continue to lock out an attacker / thief?
- Or open the doors so that the owner can climb inside quickly?

Let's Implement Our Decisions

Ignore Unlock in both other cases.

| current state S_1S_0 | ULP from ALARM | | | | | | | |
|------------------------|----------------|-----|-----|-----|-----|-----|-----|-----|
| | 000 | 001 | 011 | 010 | 110 | 111 | 101 | 100 |
| 00 | 00 | 01 | 01 | 00 | 00 | 01 | 01 | 10 |
| 01 | 01 | 01 | 01 | 00 | 00 | 01 | 01 | 01 |
| 11 | 11 | 01 | 01 | 00 | 00 | 01 | 01 | 11 |
| 10 | 10 | 01 | 01 | 00 | 00 | 01 | 01 | 11 |

from UNLOCKED

The Rest You Know How to Do


The rest is K-maps, expressions, and logic.

1. Express S_1^+ and S_0^+ in terms of S_1 , S_0 , U , L , and P .
2. Express D , R , and A in terms of S_1 , S_0 .
3. Build the combinational logic.
4. Put the next state expressions S_1^+ and S_0^+ into the D inputs of two flip-flops.


You should do it as an exercise. Break up the truth tables or use 5-variable K-maps.

One Last Tool: the Complete State Transition Diagram

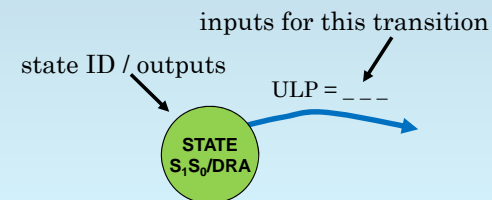The complete **state transition diagram** contains the information in both the state list and the next-state table.



Complete State Transition Diagram

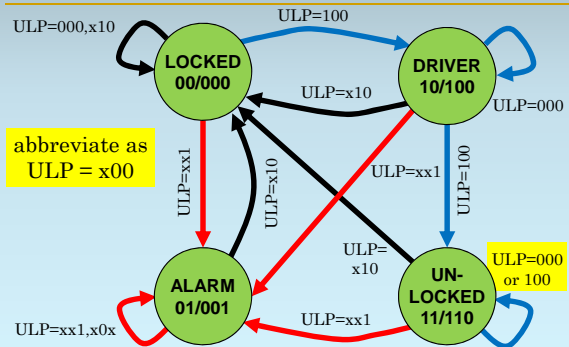

Be Careful with Input Abbreviations

Input abbreviations can render a state transition diagram

- incomplete (if labels fail to cover all input combinations), or
- inconsistent (if labels indicate multiple next states).

For example,

- self-loop from **ALARM** labeled $ULP=xx1,x0x$:
- the patterns $x01$ match both labels!
- In this case, these two combinations go to the same next state, so it's ok.